



North South University
Department of Electrical & Computer Engineering
LAB REPORT

Course Code: EEE141L

Course Title: Electrical Circuits I Lab

Course Instructor: Dr. Mohammad Abdul Matin (Mtn)

Experiment Number: 4

Experiment Name:

Delta-Wye Conversion

Experiment Date: 25/3/2021

Date of Submission: 31/3/2021

Section: 3

Submitted To: Tabia Hossain

Submitted By	Score
Student Name and ID: 1. Md. Rifat Ahmed - 1931725042	

Objectives:

- To perform Delta-Wye Conversion.
- To verify the results with measured data.
- Solve a complex circuit using Delta-Wye Conversion.

List of Equipment:

- OrCAD Software
- PSpice Simulation Software
- $5 \times 15\text{k}\Omega$ resistors
- $3 \times 5\text{k}\Omega$ resistor
- Connecting wire

Theory:

Delta-Wye Conversion:

The Delta-Wye (Δ -Y) conversion is a special technique used to handle complex circuits that cannot be handled by the usual series, parallel combinations, where we're not sure if the resistors are connected in series or parallel.

This transformation allows us to replace three resistors in a ' Δ ' configuration into a ' Y ' configuration and the other way around.

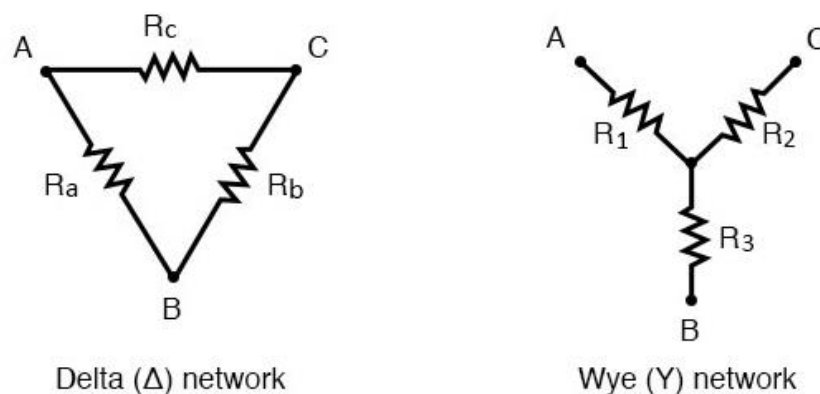


Figure: Δ -Y Network Configuration

These configurations can be redrawn to square up the resistors which is why this Δ -Y conversion is also called Pi-T (π -T) conversion.

And the π -T configurations looks like the following figure.

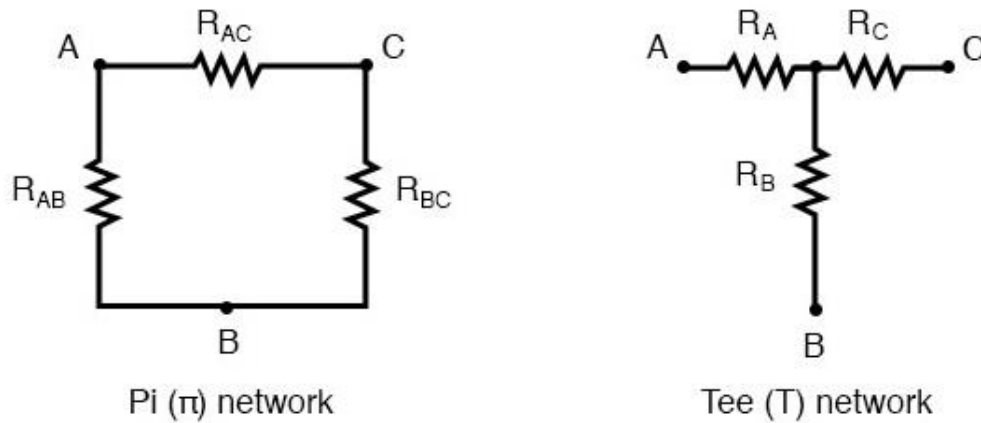


Figure: π -T Network Configuration

Delta (Δ) \rightarrow Wye (Y) Transformation:

The equations to transform a Δ network into a Y network are,

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

However, transforming a Δ network into a Y network introduces one additional node in the circuit. And these equations also apply for the π -T configuration as that's nothing but a redrawn state of the Δ -Y transformation.

Now, there's a shortcut to the Δ -Y conversion. If the Δ configuration has the three resistors with the same amount of resistance then we can calculate the resistances for Y configuration just by dividing any of the $R_a/R_b/R_c$ by 3 and that'll be the resistance of $R_1=R_2=R_3$.

$$\therefore Y = 1/3 \Delta$$

$$\Rightarrow \Delta = 3Y$$

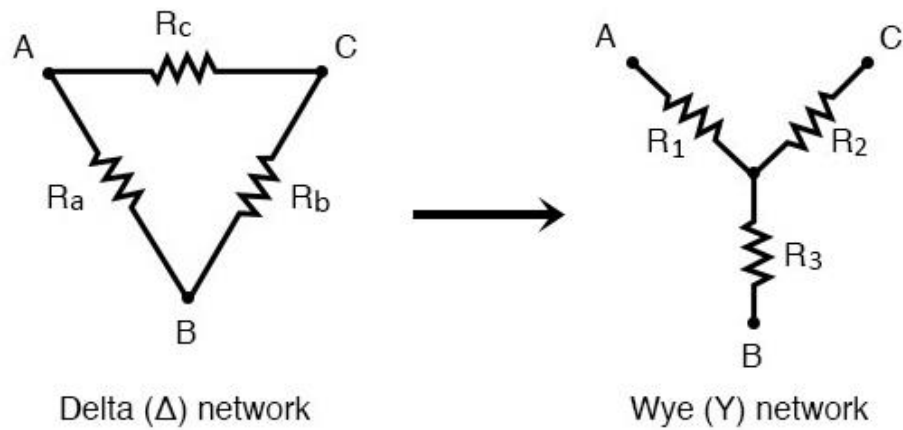


Figure: Delta (Δ) to Wye (Y) Conversion

Wye (Y) \rightarrow Delta (Δ) Transformation:

And now the equations to transform from Y configuration to Δ configuration,

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$



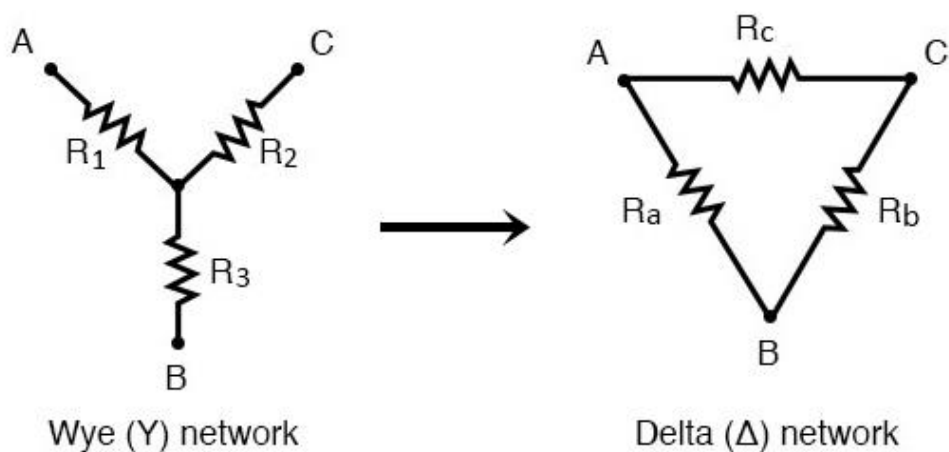


Figure: Wye (Y) to Delta (Δ) Conversion

Circuit Diagram:

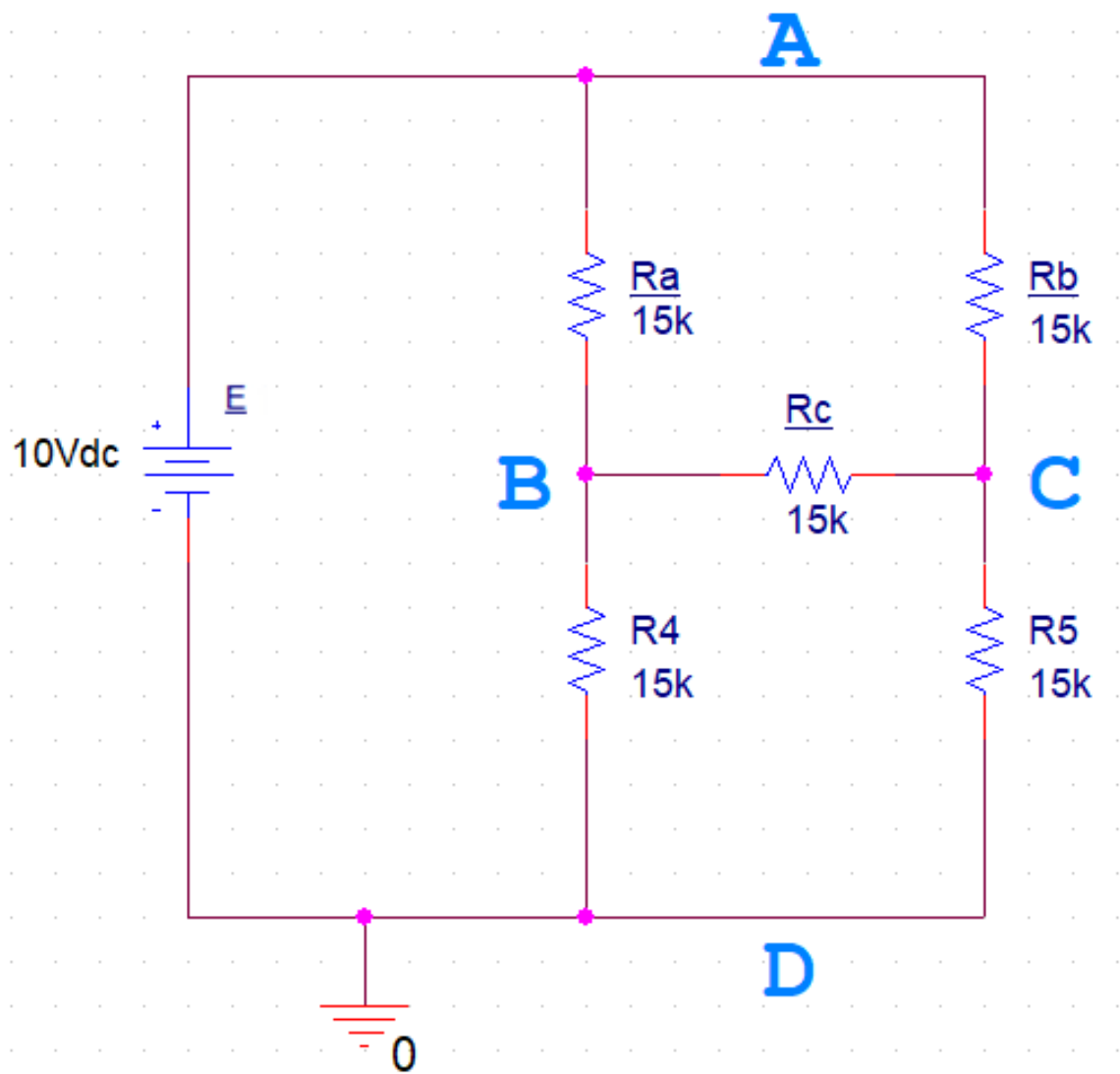

Circuit – 1

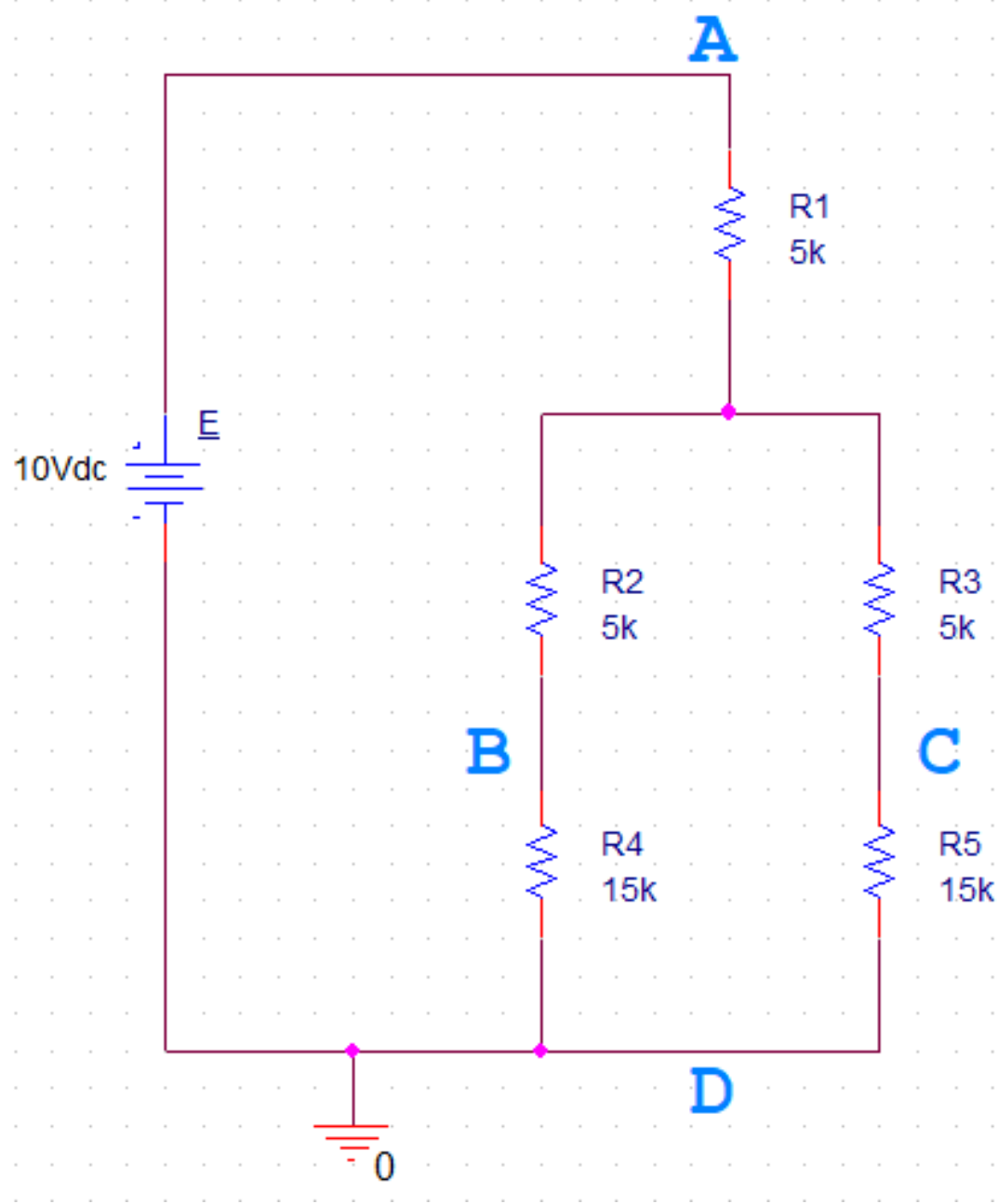

Circuit – 2

Data, Readings and Results:

Table 1:

Theoretical R	Measured R	% Error
15k	15k	0%
5k	5k	0%

Table 2:

Readings	Circuit 1	Circuit 2	% Error
V_{AD}	10V	10V	0%
V_{BD}	5V	5V	0%
V_{CD}	5V	5V	0%
V_{AB}	5V	5V	0%
V_{BC}	0V	0V	0%
V_{AC}	5V	5V	0%

Questions and Answers:

Q&A for Circuit 1:

Answer of Question 1:

The resistors in Circuit 1 are in a complex circuit which is neither series nor parallel combination.

Answer of Question 2:

I would use the Delta-Wye conversion technique to find the equivalent resistance.

Answer of Question 3:

Performing the Delta-Wye conversion for ΔABC in Circuit – 1:

Given,

$$R_a = 15\text{k}\Omega$$

$$R_b = 15\text{k}\Omega$$

$$R_c = 15\text{k}\Omega$$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{15 \times 15}{15 + 15 + 15} = 5\text{k}\Omega$$


$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c} = \frac{15 \times 15}{15 + 15 + 15} = 5\text{k}\Omega$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{15 \times 15}{15 + 15 + 15} = 5\text{k}\Omega$$

Q&A for Circuit 2:

Answer of Question 1:

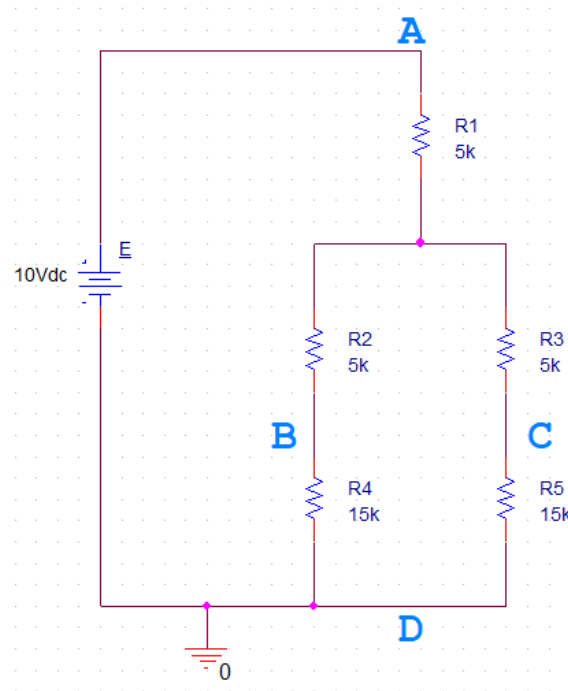Redrawing the equivalent circuit after applying the Delta-Wye conversion for ΔABC ,



And it is the same as Circuit – 2.

Answer of Question 2:

Given,

$$R_1 = 5k\Omega$$

$$R_2 = 5k\Omega$$

$$R_3 = 5k\Omega$$

$$R_4 = 15k\Omega$$

$$R_5 = 15k\Omega$$

Here, R_2 , R_4 and R_3 , R_5 are in series,

$$\therefore R_{S1} = R_2 + R_4 = 5 + 15 = 20k\Omega$$

$$\therefore R_{S2} = R_3 + R_5 = 5 + 15 = 20k\Omega$$

Now, R_{S1} and R_{S2} are in parallel,

$$\therefore R_P = R_{S1} \parallel R_{S2} = \frac{R_{S1} \times R_{S2}}{R_{S1} + R_{S2}} = \frac{20 \times 20}{20 + 20} = 10k\Omega$$

And finally, R_1 and R_P are in series,

$$\therefore R_{eq} = R_1 + R_P = 5 + 10 = 15k\Omega$$

Answer of Question 3:

Calculating the voltages for R_1 , R_2 and R_3 ,

For R_1 ,

$$V_{R1} = \frac{E \times R_1}{R_{eq}} = \frac{10 \times 5}{15} = 3.33V$$

For R_2 ,

$$V_{R2} = V_{AB} - V_{R1} = 5 - 3.33 = 1.67V$$

For R_3 ,

$$V_{R3} = V_{R2} = 1.67V$$

Answer of Question 4:

Given,

$$E = 10V$$

$$V_A = E = 10V$$

$$\begin{aligned} V_B &= E - V_{R1} - V_{R2} \\ &= 10 - 3.33 - 1.67 = 5V \end{aligned}$$

$$V_C = V_B = 5V$$

$$\begin{aligned} V_D &= E - (I_T \times R_{eq}) \\ &= E - \left(\frac{E}{R_{eq}} \times R_{eq}\right) = 10 - 10 = 0V \end{aligned}$$

$$V_{AB} = 10 - 5 = 5V$$

$$V_{BC} = 5 - 5 = 0V$$

$$V_{AC} = 10 - 5 = 5V$$

$$V_{AD} = 10 - 0 = 10V$$

$$V_{BD} = 5 - 0 = 5V$$

$$V_{CD} = 5 - 0 = 5V$$

$$\therefore \% \text{ Error for } V_{AB} = \left| \frac{\text{Experimental value} - \text{Theoretical value}}{\text{Theoretical value}} \right| \times 100\%$$

$$= \left| \frac{5-5}{5} \right| \times 100\% = 0\%$$

$$\therefore \% \text{ Error for } V_{BC} = \left| \frac{0-0}{0} \right| \times 100\% = 0\%$$

$$\therefore \% \text{ Error for } V_{AC} = \left| \frac{5-5}{5} \right| \times 100\% = 0\%$$

$$\therefore \% \text{ Error for } V_{AD} = \left| \frac{10-10}{10} \right| \times 100\% = 0\%$$

$$\therefore \% \text{ Error for } V_{BD} = \left| \frac{5-5}{5} \right| \times 100\% = 0\%$$

$$\therefore \% \text{ Error for } V_{CD} = \left| \frac{5-5}{5} \right| \times 100\% = 0\%$$

Answer of Question 5:

Using Table 2 we can clearly say that Circuit 2 is equivalent to Circuit 1. And from the percentage error column we can see that the error percentage is zero for all the readings, which indicates that both the circuit has same amount of voltages running across them for all V_{AB} , V_{BC} , V_{AC} , V_{AD} , V_{BD} and V_{CD} . So, the Delta-Wye conversion was definitely successful.

Discussion:

From this experiment we've learned the Delta-Wye conversion and Wye-Delta conversion. Using this technique, we can calculate complex circuits where the resistors connection can't be figured out. For our circuit – 1 it wasn't clear if R_a , R_b and R_c were in series or parallel but after performing Delta-Wye conversion we could easily calculate the equivalent resistance R_{eq} of our circuit. However, this conversion knowledge will not only help us for this experiment but will also help us in the future with bigger or more complex circuits. And as for the result, we got no % error which indicates that our Delta-Wye conversion was successful. And during this experiment we didn't face any problem as everything was clear and understandable during the class.