



North South University
Department of Electrical & Computer Engineering
LAB REPORT

Course Code: EEE141L

Course Title: Electrical Circuits I Lab

Course Instructor: Dr. Mohammad Abdul Matin (Mtn)

Experiment Number: 6

Experiment Name:

Verification of Thevenin's, Norton's and Maximum Power Transfer Theorem

Experiment Date: 8/4/2021

Date of Submission: 14/4/2021

Section: 3

Submitted To: Tabia Hossain

Submitted By	Score
Student Name and ID: 1. Md. Rifat Ahmed - 1931725042	

Objectives:

- Experimentally perform Thevenin's theorem, Norton's theorem and Maximum Power theorem
- Perform theoretical calculations.
- Verify the experimental values with theoretical values.

List of Equipment:

- OrCAD Software
- PSpice Software
- Resistors ($1 \times 1k\Omega$), ($1 \times 5k\Omega$), ($2 \times 10k\Omega$)
- POT ($10k\Omega$)
- Connecting Wires

Theory:

Thevenin's Theorem:

According to Thevenin's theorem we can simplify any linear circuit, no matter how complex, to an equivalent circuit with just a single voltage source and series resistance connected to a load resistance.

The Thevenin equivalent circuit has one dc voltage source called Thevenin voltage, V_{TH} and a single fixed resistor called Thevenin resistance, R_{TH} .

Norton's Theorem:

According to Norton's theorem we can simplify any linear circuit, no matter how complex, to an equivalent circuit with just a one current source and parallel resistance connected to a load resistance.

The Norton equivalent circuit has one current source called Norton Current, I_N and a single fixed resistor called Norton resistance, R_N .

Usefulness of Thevenin & Norton Theorem:

In Figure – 1 R_2 is a load resistor and if want to find the voltage and current going through it we can apply mesh analysis or nodal analysis or we can use superposition theorem but if the load resistor is not fixed and varies from time to time, we can't be doing all those calculations again and again that's where Thevenin and Norton theorem shines. We can simplify a circuit to Thevenin or Norton equivalence circuit and then just calculate everything according to the change of load resistor.


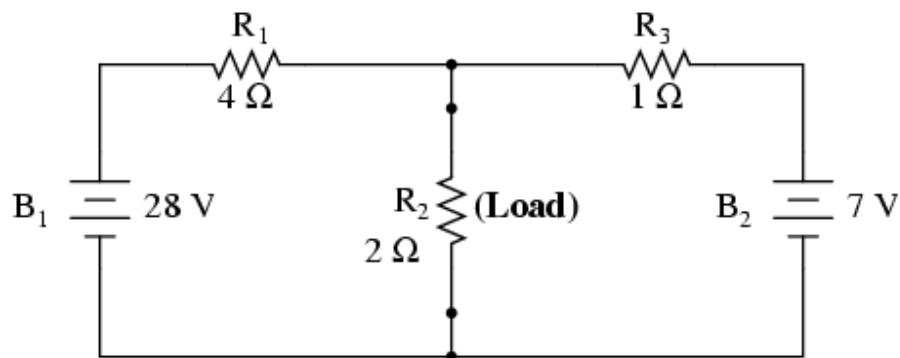


Figure – 1

Calculating the Thevenin voltage:

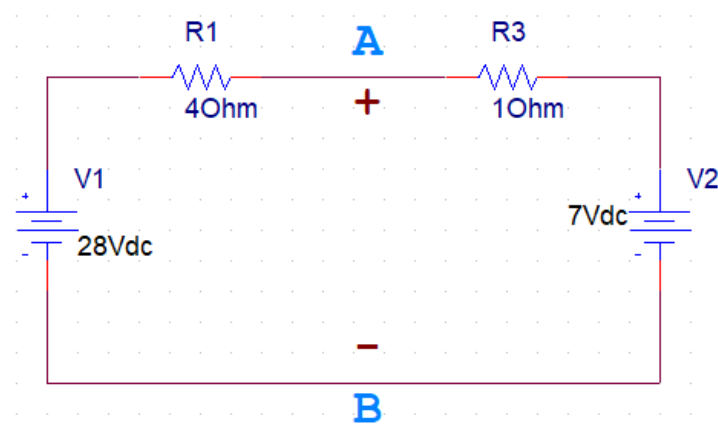
We first remove the load resistance from the circuit then calculate the open-circuit voltage at the terminals of the load resistance to calculate the Thevenin voltage of the circuit.



Calculating the Thevenin/Norton Resistance:

After removing the load resistance, we short the circuit for all the independent voltage sources and calculate the resistance at the terminals of the load resistor to get out Thevenin resistance.

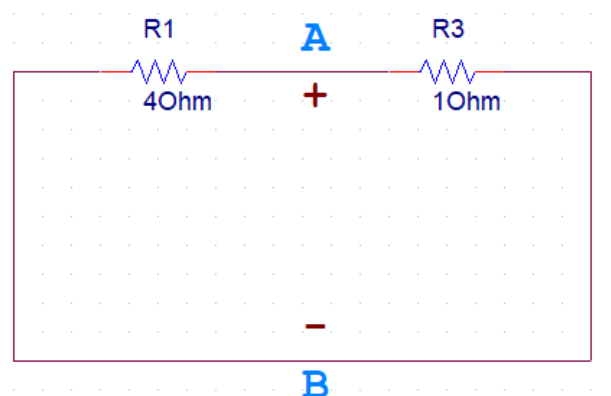And Norton resistance needs to be calculated the same way as Thevenin resistance so they're equal.




Thevenin Norton Equivalence:

Both Thevenin and Norton equivalent circuits are intended to behave the same as the original network supplying voltage and current to the load resistor. In other words, both Thevenin and Norton equivalent circuits should produce the same voltage across the load terminals with no load attached.


Thevenin and Norton resistance both needs to be calculated the same way and are equal. So,

$$R_{\text{Thevenin}} = R_{\text{Norton}}$$
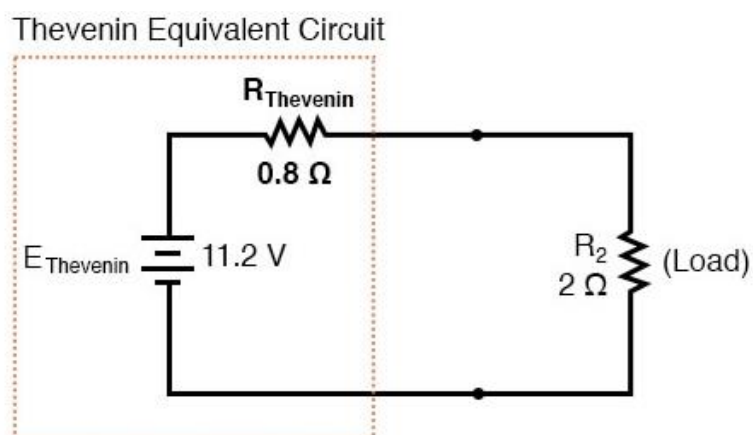
$$V_{\text{Thevenin}} = I_{\text{Norton}} R_{\text{Thevenin}}$$



Norton Equivalent Circuit

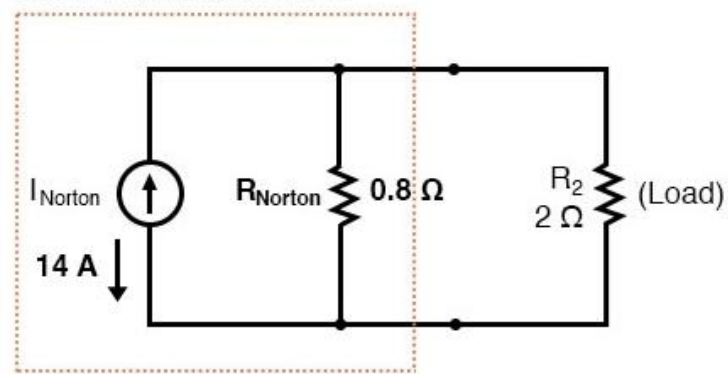

Calculating the Norton Current:

Thevenin and Norton are both equivalent circuits so to calculate Norton current, I_N we can use V_{TH} ,

$$I_{\text{Norton}} = V_{\text{Thevenin}} / R_{\text{Norton}}$$

$$\Rightarrow I_{\text{Norton}} = V_{\text{Thevenin}} / R_{\text{Thevenin}}$$

Maximum Power Theorem:

Maximum power theorem states that maximum power will be delivered to the load when that load resistance is equal to the Thevenin/Norton resistance of the network supplying the power. If the load resistance is lower or higher than the Thevenin or Norton resistance then the power dissipated will be less than maximum.

In a Thevenin or Norton Equivalent circuit,


$$I_L = V_{\text{TH}} / (R_{\text{TH}} + R_L)$$

For maximum power $R_L = R_{\text{TH}}$,


$$I_L = V_{\text{TH}} / (R_{\text{TH}} + R_{\text{TH}}) = V_{\text{TH}} / 2R_{\text{TH}}$$

$$\therefore P_{\text{Max}} = I_L^2 R_L = V_{\text{TH}}^2 / 4R_{\text{TH}}$$

Circuit Diagram:

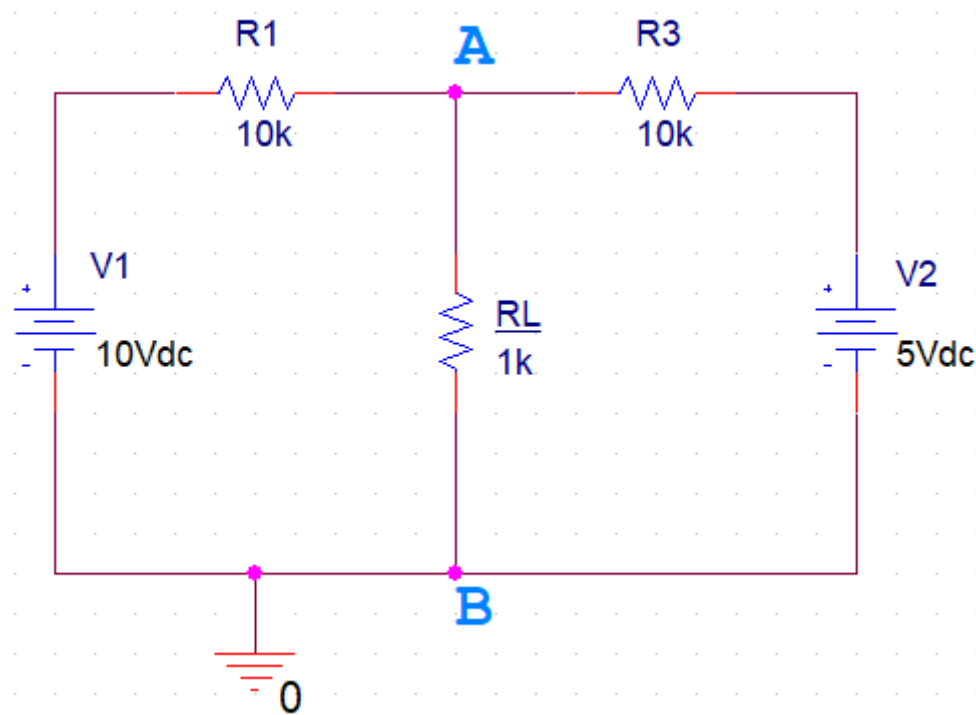

Circuit – 1

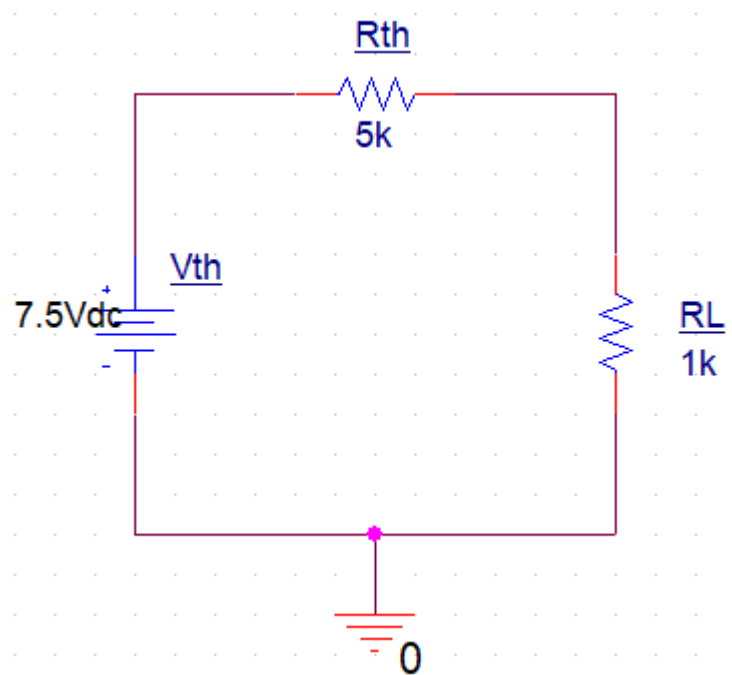

Circuit – 2

Data, Readings and Results:

Table 2:

Value	Measured	Calculated	% Error
V_L	1.25 V	1.25 V	0%
I_L	1.25 mA	1.25 mA	0%

Table 3:

Value	Measured	Calculated	% Error
V_{TH}	7.5 V	7.5 V	0%
I_N	1.5 mA	1.5 mA	0%
R_{TH}	5 k Ω	5 k Ω	0%
V_L	1.25 V	1.25 V	0%
I_L	1.25 mA	1.25 mA	0%

Table 4:

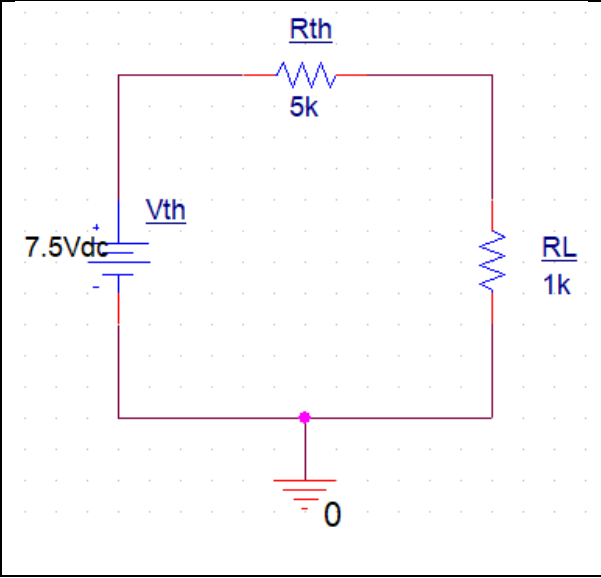
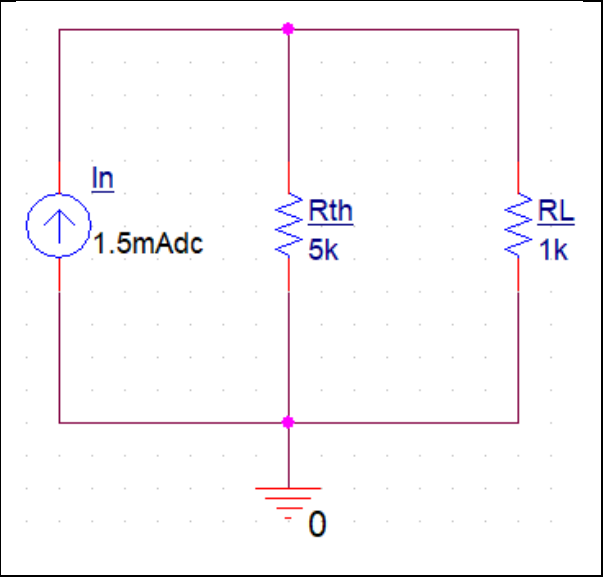
Thevenin's Equivalent Circuit	Norton's Equivalent Circuit
 <p>The diagram shows a Thevenin equivalent circuit. It consists of a DC voltage source labeled V_{th} with a value of 7.5Vdc. This source is in series with a resistor labeled R_{th} with a value of 5k. The other end of the resistor is connected to a load resistor labeled R_L with a value of 1k. The circuit is grounded at the bottom, indicated by a ground symbol and the label 0.</p>	 <p>The diagram shows a Norton equivalent circuit. It consists of a DC current source labeled I_N with a value of 1.5mA dc. This source is in parallel with a resistor labeled R_{th} with a value of 5k. The other end of the resistor is connected to a load resistor labeled R_L with a value of 1k. The circuit is grounded at the bottom, indicated by a ground symbol and the label 0.</p>

Table 5:

R_L (kΩ)	V_L (Experimental)	P_L (Experimental)	P_L (Calculated)	% Error of P_L
1	1.250 V	1.563 mW	1.563 mW	0%
2	2.143 V	2.296 mW	2.296 mW	0%
3	2.813 V	2.637 mW	2.638 mW	0.04%
4	3.333 V	2.778 mW	2.777 mW	0.04%
5	3.750 V	2.813 mW	2.813 mW	0%
6	4.091 V	2.789 mW	2.789 mW	0%
7	4.375 V	2.734 mW	2.734 mW	0%
8	4.615 V	2.663 mW	2.662 mW	0.04%
9	4.821 V	2.583 mW	2.582 mW	0.04%
10	5.000 V	2.500 mW	2.500 mW	0%

Percentage Error Calculation (For Table 5):

We've calculated all the values of P_L for different loads in Question no 7.

Now, to calculate the percentage error, we know,

Formula to calculate % Error = $\left| \frac{\text{Experimental value} - \text{Theoretical value}}{\text{Theoretical value}} \right| \times 100\%$

$$\% \text{ Error of } P_L \text{ for } 1\text{k}\Omega \text{ load} = \left| \frac{1.563 - 1.563}{1.563} \right| \times 100\% = 0\%$$

$$\% \text{ Error of } P_L \text{ for } 2\text{k}\Omega \text{ load} = \left| \frac{2.296 - 2.296}{2.296} \right| \times 100\% = 0\%$$

$$\% \text{ Error of } P_L \text{ for } 3\text{k}\Omega \text{ load} = \left| \frac{2.637 - 2.638}{2.638} \right| \times 100\% = 0.04\%$$

$$\% \text{ Error of } P_L \text{ for } 4\text{k}\Omega \text{ load} = \left| \frac{2.778 - 2.777}{2.777} \right| \times 100\% = 0.04\%$$

$$\% \text{ Error of } P_L \text{ for } 5\text{k}\Omega \text{ load} = \left| \frac{2.813 - 2.813}{2.813} \right| \times 100\% = 0\%$$

$$\% \text{ Error of } P_L \text{ for } 6\text{k}\Omega \text{ load} = \left| \frac{2.789 - 2.789}{2.789} \right| \times 100\% = 0\%$$

$$\% \text{ Error of } P_L \text{ for } 7\text{k}\Omega \text{ load} = \left| \frac{2.734 - 2.734}{2.734} \right| \times 100\% = 0\%$$

$$\% \text{ Error of } P_L \text{ for } 8\text{k}\Omega \text{ load} = \left| \frac{2.663 - 2.662}{2.662} \right| \times 100\% = 0.04\%$$

$$\% \text{ Error of } P_L \text{ for } 9\text{k}\Omega \text{ load} = \left| \frac{2.583 - 2.582}{2.582} \right| \times 100\% = 0.04\%$$

$$\% \text{ Error of } P_L \text{ for } 10\text{k}\Omega \text{ load} = \left| \frac{2.500 - 2.500}{2.500} \right| \times 100\% = 0\%$$

Graphical Analysis:

Roll No.



Fig: P_L vs R_L Graph

The P_L vs R_L graph above is drawn using the data from Table 5. In this graph as we increased the load the value of P_L was also increasing until it reached the peak where we got the maximum power and at that point R_L was $5k\Omega$. So, the peak point was for $5k\Omega$ load where we got $P_L = 2.813 \text{ mW}$. And then the power started to decline as we increased the load.

So according to the power theorem we'll get the maximum power when R_L is equal to R_{TH} and in this graph we can clearly see that happening as the power was increasing at first and reached the maximum point where $R_L = 5k\Omega = R_{TH}$ and then P_L started to decrease so we can say that the graph satisfies the maximum power theorem.

Questions and Answers:

Answer of Question 1:

Calculating the theoretical values for Table 2,

Applying nodal analysis at Node A of circuit – 1 to get V_L ,

$$\begin{aligned}(V_L - 10)/10 + V_L/1 + (V_L - 5)/10 &= 0 \\ \Rightarrow (V_L/10) - 1 + V_L + (V_L/10) - 0.5 &= 0 \\ \Rightarrow V_L/10 + V_L + V_L/10 &= 1.5 \\ \Rightarrow \frac{V_L + 10V_L + V_L}{10} &= 1.5 \\ \Rightarrow 12V_L &= 15 \\ \therefore V_L &= 1.25 \text{ V}\end{aligned}$$

$$\begin{aligned}\text{Now, } I_L &= V_L / R_L \\ \Rightarrow I_L &= 1.25\text{V} / 1\text{k}\Omega \\ \therefore I_L &= 1.25 \text{ mA}\end{aligned}$$


$$\begin{aligned}\% \text{ Error for } I_L &= \left| \frac{\text{Experimental value} - \text{Theoretical value}}{\text{Theoretical value}} \right| \times 100\% \\ &= \left| \frac{1.25 - 1.25}{1.25} \right| \times 100\% \\ &= 0\%\end{aligned}$$

$$\begin{aligned}\& \% \text{ Error for } V_L &= \left| \frac{\text{Experimental value} - \text{Theoretical value}}{\text{Theoretical value}} \right| \times 100\% \\ &= \left| \frac{1.25 - 1.25}{1.25} \right| \times 100\% \\ &= 0\%\end{aligned}$$

Answer of Question 2:

Calculating the theoretical values for Table 3 using Thevenin's and Norton's theorem,

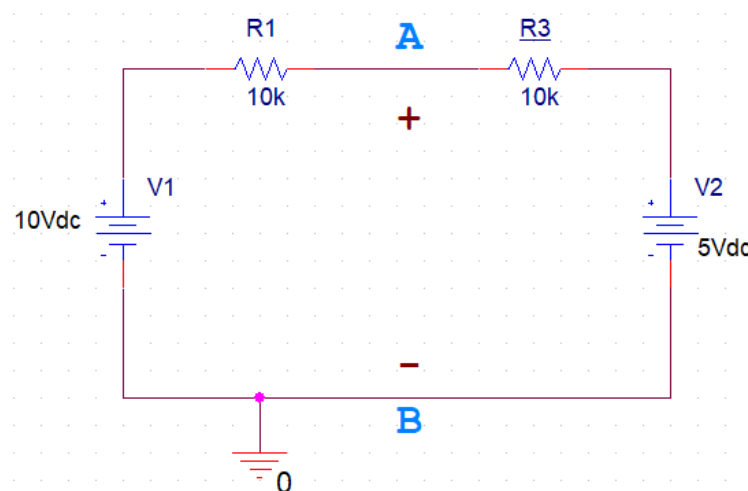Removing the Load Resistor and applying nodal analysis at Node A to get V_{TH} ,



$$\begin{aligned}(V_{TH} - 10)/10 + (V_{TH} - 5)/10 &= 0 \\ \Rightarrow (V_{TH}/10) - 1 + (V_{TH}/10) - 0.5 &= 0 \\ \Rightarrow V_{TH}/5 &= 1.5 \\ \therefore V_{TH} &= 7.5 \text{ V}\end{aligned}$$

Now, the two 10k Ω resistors are in parallel,

$$\therefore R_{TH} = \frac{10 \times 10}{10 + 10} = 5 \text{ k}\Omega$$

$$\begin{aligned}\text{So, } I_N &= V_{TH} / R_{TH} \\ \Rightarrow I_N &= 7.5 \text{ V} / 5 \text{ k}\Omega \\ \therefore I_N &= 1.5 \text{ mA}\end{aligned}$$

$$\begin{aligned}I_L &= V_{TH} / (R_L + R_{TH}) \\ \Rightarrow I_L &= 7.5 \text{ V} / (1 + 5) \text{ k}\Omega \\ \therefore I_L &= 1.25 \text{ mA}\end{aligned}$$

$$\begin{aligned}V_L &= I_L R_L \\ \Rightarrow V_L &= 1.25 \text{ mA} \times 1 \text{ k}\Omega \\ \therefore V_L &= 1.25 \text{ V}\end{aligned}$$

Formula to calculate % error is = $\left| \frac{\text{Experimental value} - \text{Theoretical value}}{\text{Theoretical value}} \right| \times 100\%$

$$\therefore \% \text{ Error for } V_{TH} = \left| \frac{7.5 - 7.5}{7.5} \right| \times 100\% = 0\%$$

$$\% \text{ Error for } I_N = \left| \frac{1.5 - 1.5}{1.5} \right| \times 100\% = 0\%$$

$$\% \text{ Error for } R_{TH} = \left| \frac{5 - 5}{5} \right| \times 100\% = 0\%$$

$$\% \text{ Error for } I_L = \left| \frac{1.25 - 1.25}{1.25} \right| \times 100\% = 0\%$$

$$\& \% \text{ Error for } V_L = \left| \frac{1.25 - 1.25}{1.25} \right| \times 100\% = 0\%$$

Here, we can see that the percentage error for all V_{TH} , R_{TH} , I_N , I_L , V_L is zero. Which means that the experimental values of all these are exactly the same as the theoretical values that we calculated using Thevenin's and Norton's theorem which indicates that the Thevenin's and Norton's theorem stands for our experimental values. So, Thevenin's and Norton's theorem is verified.

Answer of Question 3:

We know that both Thevenin and Norton circuit produces the same result. And the equivalence relation between these two theorems can be denoted as,

$$\begin{aligned} R_N &= R_{TH} \\ \Rightarrow V_{TH} &= I_N R_N = I_N R_{TH} \end{aligned}$$

So, the voltage drop at the load resistor for both theorems should be same if the circuits are equivalent as they're always going to produce the same result for different values of the load resistor.

Now, if we take a look at table 3, we can see that the load resistor has a voltage drop of 1.25 V for the Thevenin circuit so if both the theorem are equivalent then for Norton equivalent circuit the voltage drop at the load resistor should be same.

$$\begin{aligned} V_L &= I_L R_L = \frac{R_{TH}}{R_{TH} + R_L} \times I_N \times R_L \\ \Rightarrow V_L &= \frac{5}{5 + 1} \times 1.5 \times 1 \\ \therefore V_L &= 1.25 \text{ V} \end{aligned}$$

The value of the voltage drop at the load resistor is same for both the circuit so, this proves that the Thevenin and Norton are equivalent circuit. (Proved)

Answer of Question 4:

The Graph is Drawn in the Graphical Analysis section above.

Answer of Question 5:

From the graph we can see that for $R_L = 5k\Omega$ we get the maximum power.

Answer of Question 6:

From Question no 3 we get,

$$V_{TH} = 7.5 \text{ V}$$

$$R_{TH} = 5k\Omega$$

Maximum Power,

$$P_{Max} = V_{TH}^2 / 4 R_{TH}$$

$$\Rightarrow P_{Max} = (7.5V)^2 / (4 \times 5k\Omega)$$

$$\therefore P_{Max} = 2.813 \text{ mW}$$

Answer of Question 7:

Verifying the maximum power theorem:

According to the maximum power theorem, maximum power will be delivered to the load when that load resistance is equal to the Thevenin/Norton resistance of the network supplying the power. So, when $R_L = R_{TH}$ we'll get the maximum power P_{Max} . So, the maximum power theorem will be verified if the power we get for higher or lower load is less than what we get when $R_L = R_{TH}$.

From Q3 we get, $R_{TH} = 5k\Omega$ so power should be max for $R_L = 5k\Omega$.

Now, P for $1k\Omega$ load,

$$V_L = \frac{1}{1+5} \times 7.5$$

$$\therefore V_L = 1.250 \text{ V}$$

$$P = V_L^2 / R_L = (1.250)^2 / 1\text{k}\Omega$$

$$\therefore P = 1.563 \text{ mW}$$

Now, P for 2k Ω load,

$$V_L = \frac{2}{2+5} \times 7.5$$

$$\therefore V_L = 2.143 \text{ V}$$

$$P = V_L^2 / R_L = (2.143)^2 / 2\text{k}\Omega$$

$$\therefore P = 2.296 \text{ mW}$$

Now, P for 3k Ω load,

$$V_L = \frac{3}{3+5} \times 7.5$$

$$\therefore V_L = 2.813 \text{ V}$$

$$P = V_L^2 / R_L = (2.813)^2 / 3\text{k}\Omega$$

$$\therefore P = 2.638 \text{ mW}$$

P for 4k Ω load,

$$V_L = \frac{4}{4+5} \times 7.5$$

$$\therefore V_L = 3.333 \text{ V}$$

$$P = V_L^2 / R_L = (3.333\text{V})^2 / 4\text{k}\Omega$$

$$\therefore P = 2.777 \text{ mW}$$

Now, P for 5k Ω load,

$$V_L = \frac{5}{5+5} \times 7.5$$

$$\therefore V_L = 3.750 \text{ V}$$

$$P = V_L^2 / R_L = (3.750)^2 / 5\text{k}\Omega$$

$$\therefore P = 2.813 \text{ mW}$$

Now, P for 6k Ω load,

$$V_L = \frac{6}{6+5} \times 7.5$$

$$\therefore V_L = 4.091 \text{ V}$$

$$P = V_L^2 / R_L = (4.091 \text{ V})^2 / 6\text{k}\Omega$$

$$\therefore P = 2.789 \text{ mW}$$

Now, P for 7kΩ load,

$$V_L = \frac{7}{7+5} \times 7.5$$

$$\therefore V_L = 4.375 \text{ V}$$

$$P = V_L^2 / R_L = (4.375)^2 / 7\text{k}\Omega$$

$$\therefore P = 2.734 \text{ mW}$$

Now, P for 8kΩ load,

$$V_L = \frac{8}{8+5} \times 7.5$$

$$\therefore V_L = 4.615 \text{ V}$$

$$P = V_L^2 / R_L = (4.615)^2 / 8\text{k}\Omega$$

$$\therefore P = 2.662 \text{ mW}$$

Now, P for 9kΩ load,

$$V_L = \frac{9}{9+5} \times 7.5$$

$$\therefore V_L = 4.821 \text{ V}$$

$$P = V_L^2 / R_L = (4.821)^2 / 9\text{k}\Omega$$

$$\therefore P = 2.582 \text{ mW}$$

Now, P for 10kΩ load,

$$V_L = \frac{10}{10+5} \times 7.5$$

$$\therefore V_L = 5.000 \text{ V}$$

$$P = V_L^2 / R_L = (5.000)^2 / 10\text{k}\Omega$$

$$\therefore P = 2.500 \text{ mW}$$

Here, we can see that the values of P starts to increase as we increase the load but when it equals to the Thevenin resistance, R_{TH} we get the maximum value of P (P_{Max}) and then the value of P starts to fall.

So, we get the maximum power when the load is equal to the Thevenin resistance which is what the maximum power theorem says.

\therefore Maximum Power theorem is verified.

Discussion:

From this experiment we've learned three new theorems – Thevenin's, Norton's and Maximum Power theorem. We can use Thevenin or Norton's theorem to simplify any linear circuit to an equivalent circuit that has only one voltage source in case of Thevenin's and only one current source in case of Norton's and one single fixed resistor and a load resistor connected in series for Thevenin's and in parallel for Norton's theorem. This is a great way to simplify a complex circuit. And finally, from the maximum power theorem we learned how to calculate the maximum power a circuit can reach. As for the result of our experiment, the percentage of error we got was very low, zero for some and close to zero for some, meaning that our experiment was done correctly. However, during this experiment it got a bit confusing working with three new theorems at the same time so had to go through the manual and recording a few times to clear things other than that everything was good.